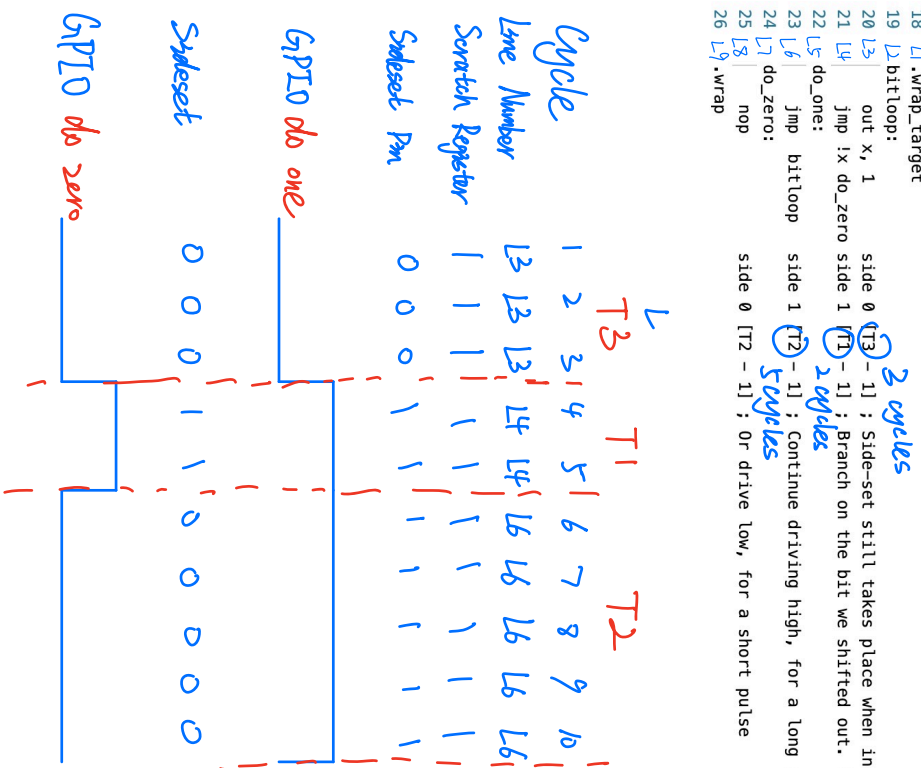


```

18 L1.wrap_target
19 L2.bitloop:
20 L3 | out x, 1 | side 0 [T3 - 1] ; Side-set still takes place when instruction stalls
21 L4 | jmp ix do_zero side 1 [T1 - 1] ; Branch on the bit we shifted out. Positive pulse
22 L5 do_one:
23 L6 | jmp bitloop | side 1 [T2 - 1] ; Continue driving high, for a long pulse
24 L7 do_zero:
25 L8 | nop | side 0 [T2 - 1] ; Or drive low, for a short pulse
26 L9.wrap

```




SM cycle count  
SM clock signal

GPIO output pin voltage

MSB Serial Input pin voltage

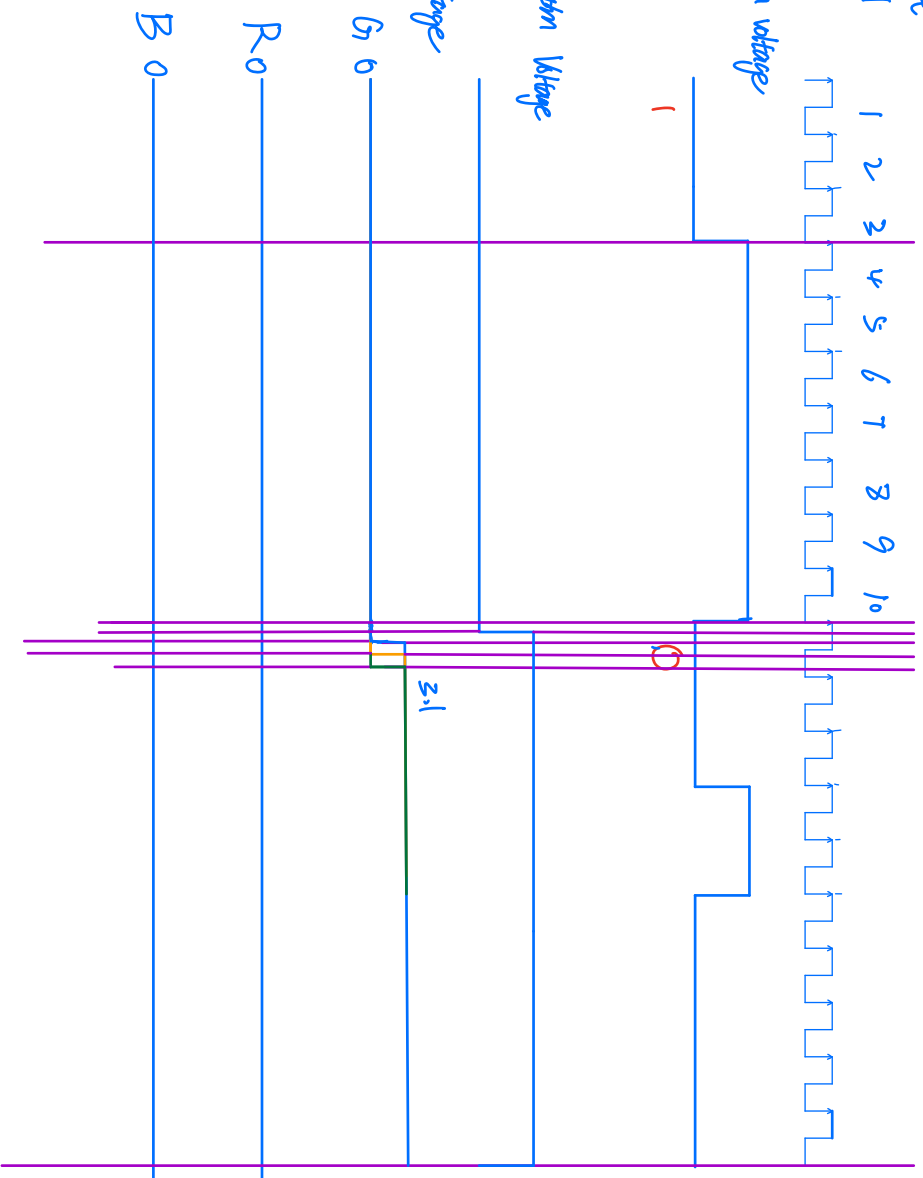LED supply voltage  
LED current  
APDS 9960



...

...

...

...

SM cycle count  
SM clock signal

71

81

91

GPIO output pin voltage

0

1

0

VB312 Serial Input pin voltage

LED supply voltage  
LED current  
APDS 9960


3.1

R

G


2

B 0

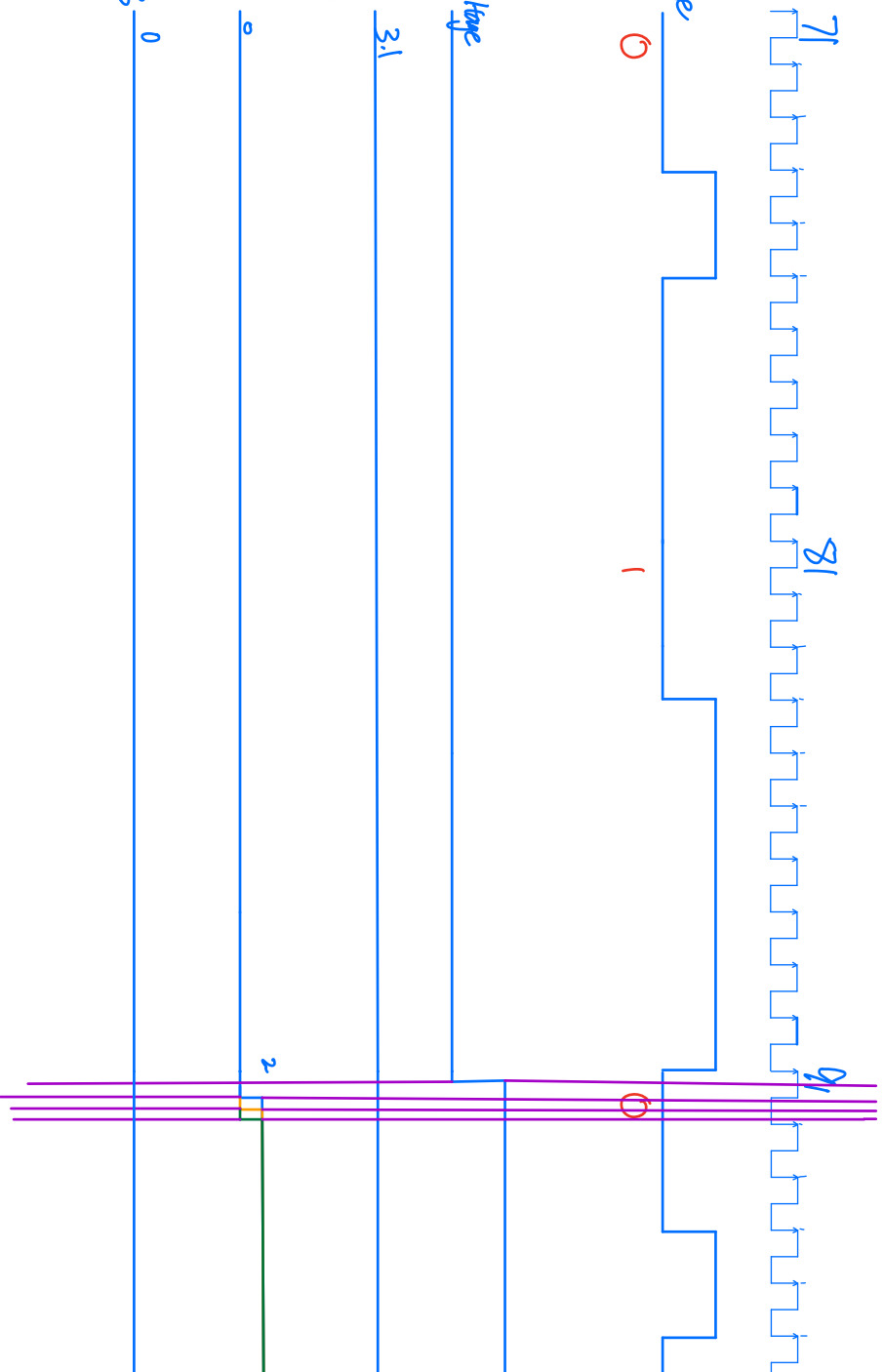




...

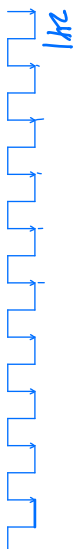

...



...

 

...



...



...

